

Complex impedance analysis and relationships with electrical conductivity, and dielectric constants

Fathy Salman

Physics department, Faculty of Science, Banha University,
 Egypt

Introduction

AC impedance spectroscopy is a valuable tool for studying both the bulk transport properties of a material and the ac conductivity and the dielectric properties. The principle of the impedance analysis method is based on measurements of the sample impedance taken over a wide range of frequencies and then analysed in the complex impedance plane. The method was firstly applied to solid electrolytes problems by Bauerle⁽¹⁹⁾ and then used by many workers for various superionic conductors. The impedance analysis method requires the determination from the measurements two parts of the complex impedance of the sample $Z^* = Z' + j Z''$. The main parameters R and C are deduced from the analysis of impedance method

Theoretical background:

The impedance is defined as the Z is the complex ratio of the applied (ac) voltage V (ω) to the resultant current I(ω) at frequency ω

$$Z = \frac{V(\omega)}{I(\omega)} \quad (1)$$

The impedance is most directly interpreted when written in polar form, can be expressed in terms of the the modulus |Z| and the phase angle ϕ

$$Z^* = V^* / I^* = |Z| e^{j\phi} \quad (2)$$

Where the magnitude |Z| represents the ratio of the voltage difference amplitude to the current amplitude, while the argument ϕ gives the phase difference between voltage and current and j is the imaginary unit.

Using Euler's relationship:

$$Z^* = |Z| \cos\phi + j|Z| \sin\phi \quad (3)$$

The impedance is then expressed as

$$Z^* = Z' + j Z'' \quad (4)$$

$$\begin{aligned} Z' &= |Z| \cos\phi \\ Z'' &= |Z| \sin\phi \end{aligned} \quad (5) \quad (6)$$

~~The main parameters deduced from the analysis of impedance method are R and C~~

In Cartesian form Z^* is defined as

$$Z^* = V^* / I^* = R + j X \quad (7)$$

where the real part of impedance is the resistance R and the imaginary part is the reactance X. In case of a capacitor $Z_c = 1/j\omega C$ i.e. $X = X_c = (-1/\omega C)$. The capacitor is a result of the sample's geometry, while the resistor represents the resistivity of the bulk. This impedance depends on the frequency and is entirely capacitive.

$$Z^* = R + j(-1/\omega C) \quad (8)$$

From above relations we obtain :

$$R = Z' \quad (9)$$

$$-1/\omega C = Z''$$

$$C = -1/\omega Z''$$

(10)

$$\tan \phi = Z'' / Z'$$

$$\text{Or } \tan \delta = Z' / Z'' \quad (11)$$

Table

F (Hz)	Z (Ohm)	Q	Z' = Z cos ϕ	Z'' = Z sin ϕ	C = 1/ $\omega Z''$	R = z'	tan $\delta = z' / z''$
-	-	--					

Data Presentation

Complex Impedance Plot

If the real part Z' is plotted on the x-axis and the imaginary part Z'' on the y-axis of a chart, a so called "Nyquist plot," or complex plane impedance diagram, is revealed. As shown

in Figure , this plot has the shape of a semicircle. Notice that in this plot the y-axis was chosen as negative notation and that each

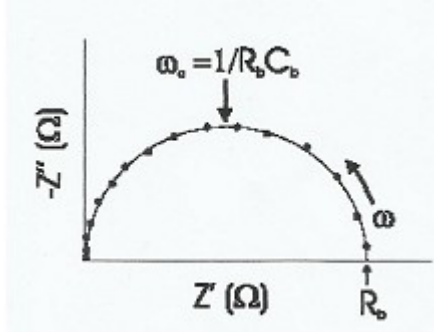


Figure 1. Nyquist Plot with Impedance Vector

point on the Nyquist plot is the impedance at one frequency [1]. On the Nyquist plot the impedance can be represented as a vector of length $|Z|$. The angle between this vector and the x-axis is φ , or "phase angle" which also has a negative notation, as (from Eq. 1-11):

There is a parameter $\tau=RC$ called "time constant," which is associated with this circuit, and a corresponding "characteristic circular" frequency $\omega_c= 1/\tau$ and "characteristic" or "critical relaxation" frequency. At very high frequencies the impedance is completely capacitive, while at low frequencies it becomes completely resistive and approaches the value of R , which equals the diameter of the Nyquist plot semicircle. The phase angle φ tends towards -90° at high frequency and towards 0° at low frequency, and critical frequency f_c corresponds to a midpoint transition where the phase angle is -45° and $Z' = Z'' = R/2$. The diameter of the semicircle is taken as the bulk resistance. Then

$$\sigma_b = \frac{1}{R_b} \cdot \frac{t}{a}$$

The Nyquist Plot in Figure 1 results from the electrical circuit of Figure 2. The semicircle is characteristic of a single "time constant". Impedance plots often contain several semicircles. Often only a portion of a semicircle is seen.

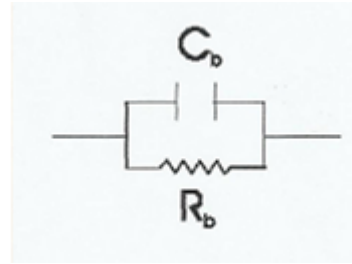


Figure 2. Simple Equivalent Circuit with One Time Constant

Another popular presentation method is the Bode Plot. The impedance is plotted with log frequency on the X-axis and both the absolute values of the impedance ($|Z|=Z_0$) and the phase-shift on the Y-axis. Unlike the Nyquist Plot, the Bode Plot does show frequency information.

Ac conductivity $\sigma(\omega)$ is calculated by using the relation,

$$\sigma(\omega) = \frac{1}{R} \times \frac{t}{a}$$

where R is the resistance, t and a are the thickness and the area

Dielectric constant ϵ' is calculated using the following relation:

$$\epsilon' = \frac{C}{\epsilon_0} \times \frac{t}{a}$$

where C is the capacitance $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$, t and a are the thickness and the area.

Dielectric Loss ϵ'' is calculated using the following relation:

$$\epsilon'' = \epsilon' \tan \delta$$

where $\delta = (90 - \varphi)$, φ is the phase angle.

Conclusions

Complex impedance analysis and relationships with electrical conductivity, and dielectric constants

The impedance measurements of the sample is taken in terms of the the modulus $|Z|$ and the phase angle ϕ taken over a wide range of frequencies. The values of Z' and Z'' can be found ,R and C are deduced. Ac conductivity $\sigma(\omega)$, dielectri constant ϵ' and dielectric Loss ϵ'' are determined.

References

The following sources were used in preparing this application note
 Bauerle J E 1069 *J Phys. Chem. Solids* **30** 2657.
 Mackdonald J R (ed) 1987. Impedance spectroscopy emphasizing solid state materials and systems (New York Wiley).

The Equivalent Circuit of Impedance

The simplest model for an electrode – sample system under an applied voltage is a capacitor and resistor in parall. Figure a. The capacitor is a result of the sample’s geometry, while the resistor represents the resistivity of the bulk. The impedance of such circuit at frequency ω consists of the real part R and **the imaginary part $1/\omega c$ and is written as :**

$$\frac{1}{Z} = \frac{1}{R} + j\omega c$$

The value Z can put in the form ;

$$Z = R \left[\frac{1 - j\omega\tau}{1 + \omega^2\tau^2} \right]$$

Which can be separated into the real part Z' and the imaginary part Z'' as :

$$Z' = \frac{R\omega\tau}{1 + \omega^2\tau^2}$$

$$Z'' = \frac{R}{1 + \omega^2\tau^2}$$

By ellimainating ω these two equations (1.10) and (1.11) can be combined and written in the form of a circle :

$$Z'^2 - Z' R + Z''^2 = 0$$

Adding $R^2/4$ to both sides of equation (1.12) one obtains

$$(Z' - \frac{1}{2} R)^2 + Z''^2 = (\frac{1}{2} R)^2$$

Comparing this equation with the standard form of the equation of a circle , one can see that the Z-plane plot is a semicircle in the first quadrant with center at $(\frac{1}{2} R, 0)$ and with a radius $\frac{1}{2} R$ fig 3.1.b. It can be shown also that at the maxium of the semicircle $\omega\tau = 1$ where $\tau = RC$ is the time constant or the relaxation time of the circuit .

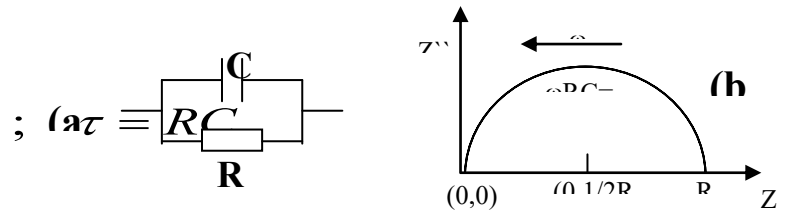


Figure (1) : Complex impedance plot for the parallel circuit RC .

So, when from the complex impedance measurements when only one semicircle obtained and this semicircle originates in the (0,0) point ,it means that only one resistance R and one capacity c both parallel combined , can be described to the sample in such a case, these should be the bulk resistance and capacity of the sample .

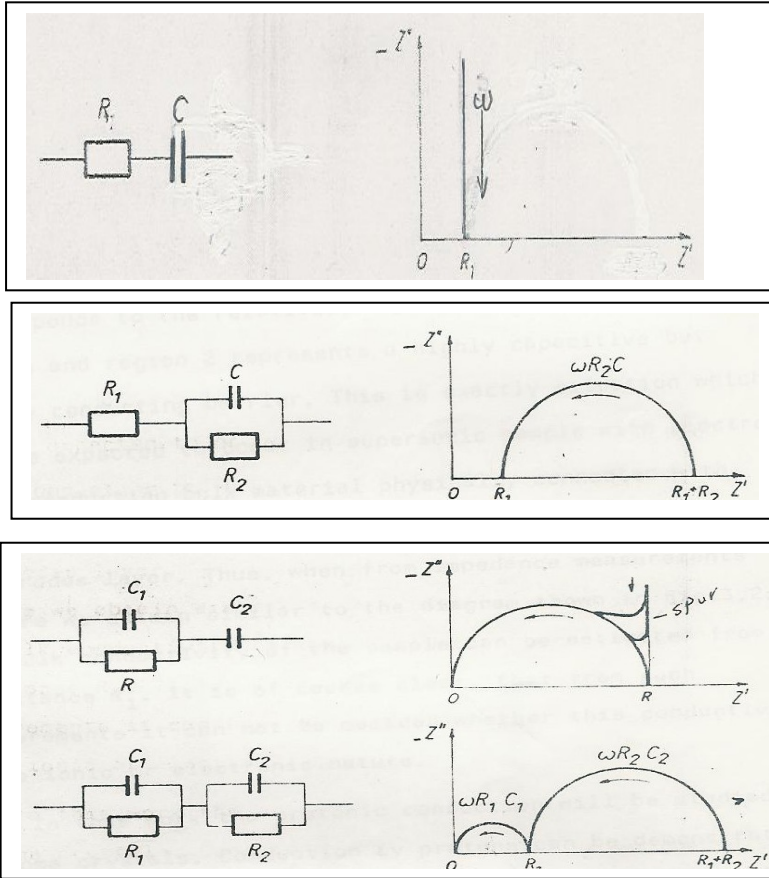


Figure (2,3,4&5) : Complex impedance plots for simple circuits RC of different combinations a, b c, d, e, f and g respectively.

Nyquist and Bode representation of complex impedance data for ideal electrical circuits

(Nyquist Plot)

The impedance analysis method requires the determination from the measurements at each frequency f two parts of the impedance: the real part Z' and the imaginary part Z'' . The real